ELECTRONIC CIRCUIT

Write the words under the pictures.


switch / battery / wire / bulb



.....



.....

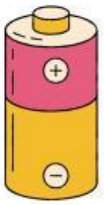


.....



.....

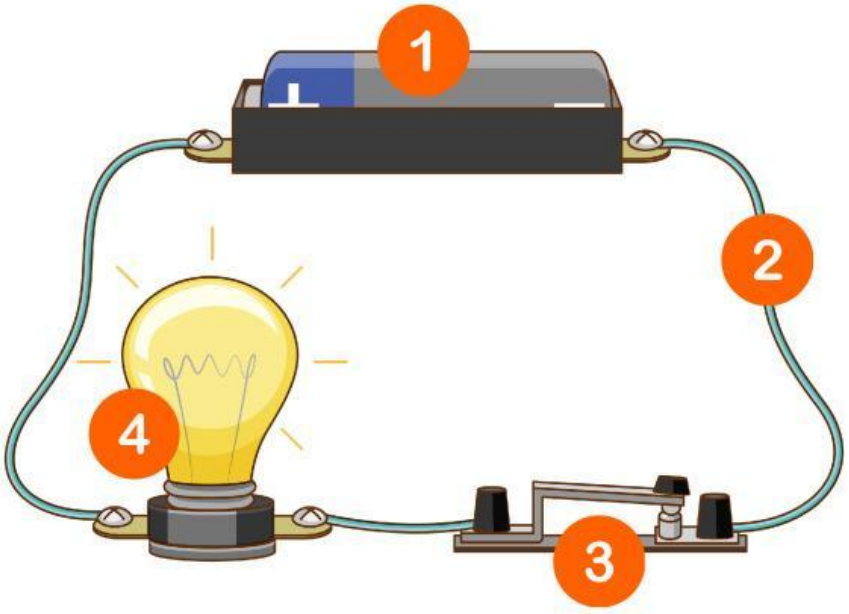Write the components of the electronic circuit below.



1- .....

2- .....

3- .....

4- .....

LIVEWORKSHEETS