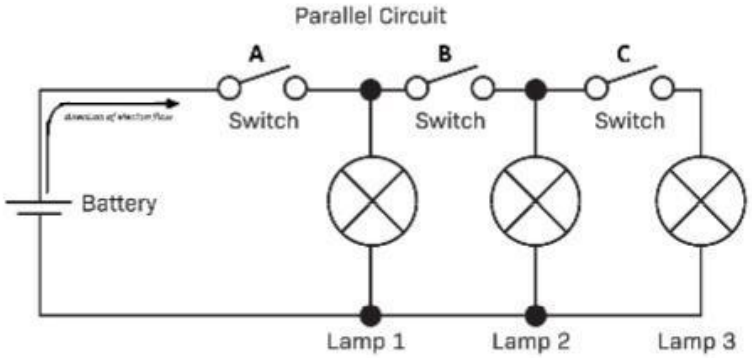


If just Lamp 1 is going to be on which switches should be closed, and which should be opened.

Switch A Open Closed **Switch B Open Closed** **Switch C Open Closed**

LIVEWORKSHEETS