
Series and Parallel Circuits

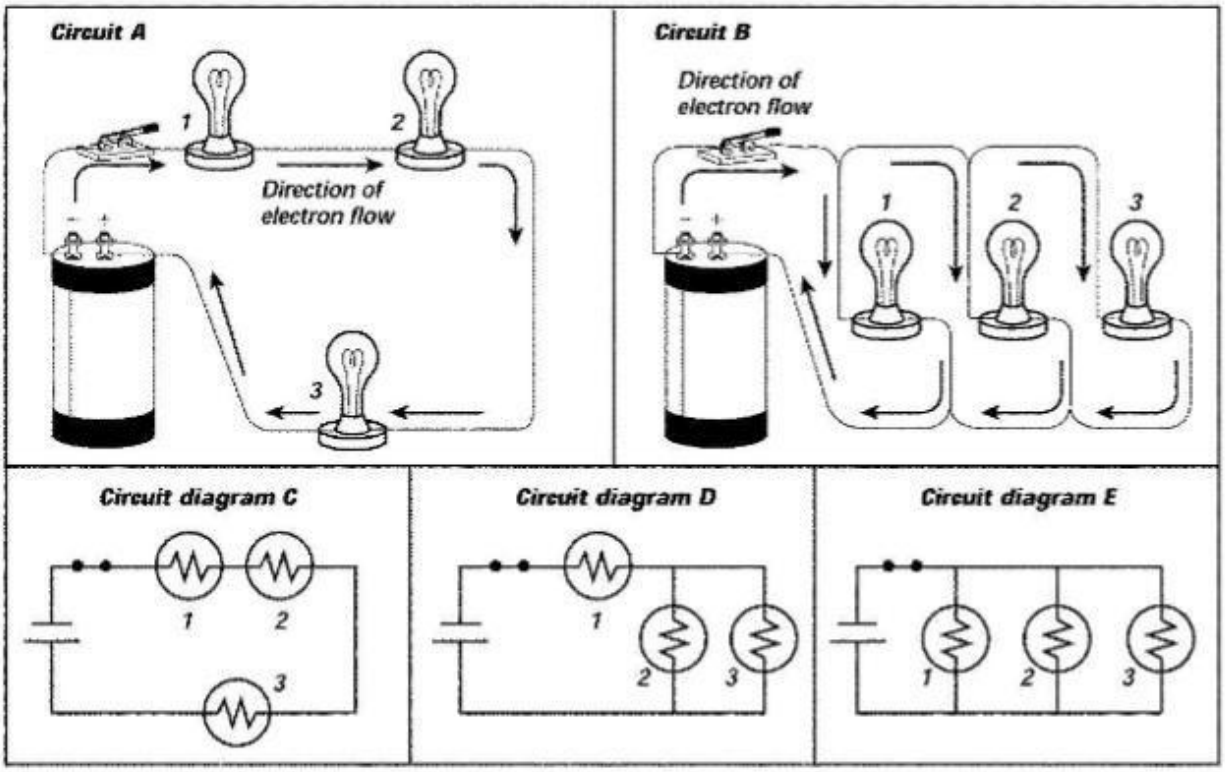

Match the Circuit A and Circuit B with the correct Circuit diagram C, D, or E

Circuit A Diagram matches

Circuit B Diagram matches

LIVEWORKSHEETS