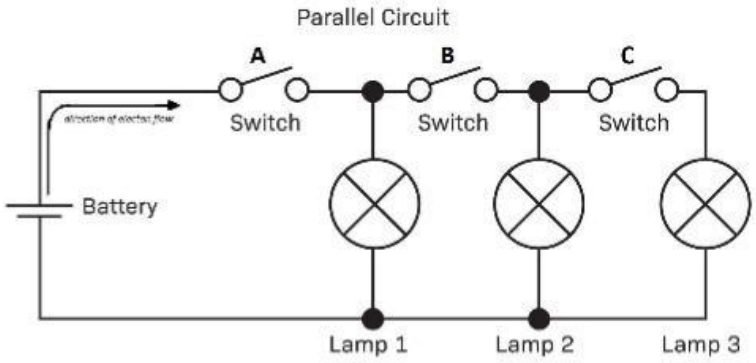


In order for just Lamp 3 to be off which switches should be opened and which should be closed?

Switch A Open Closed **Switch B Open Closed** **Switch C Open Closed**

LIVEWORKSHEETS