
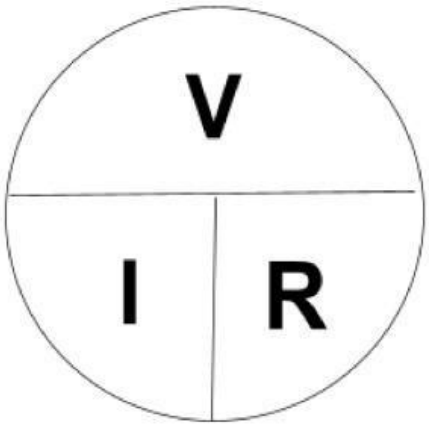


What is the correct equation for the Voltage in Volts?

What is the correct equation for Current in Amps?

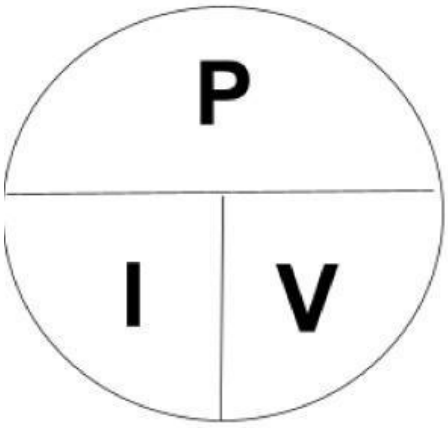
What is the correct equation for Resistance in Ohms (Ω)?




What is the correct equation for Power in Watts?

What is the correct equation for Current in Amps?

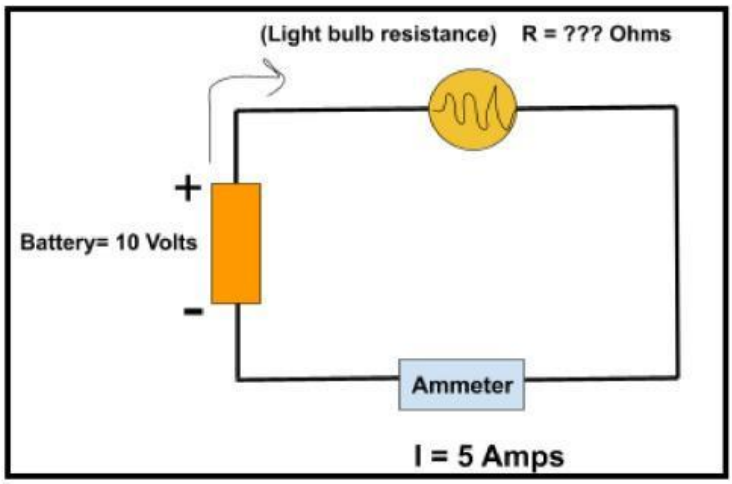
What is the correct equation for the Voltage in Volts?



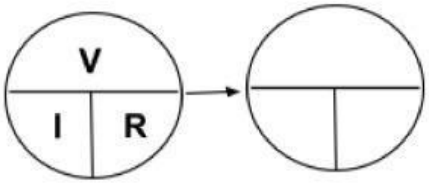
What is the resistance of the light bulb in ohms?




What is the power output of the battery?

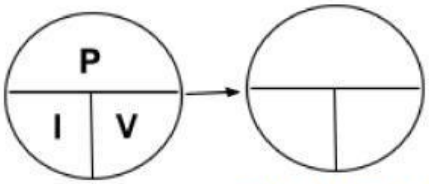


LIVEWORKSHEETS

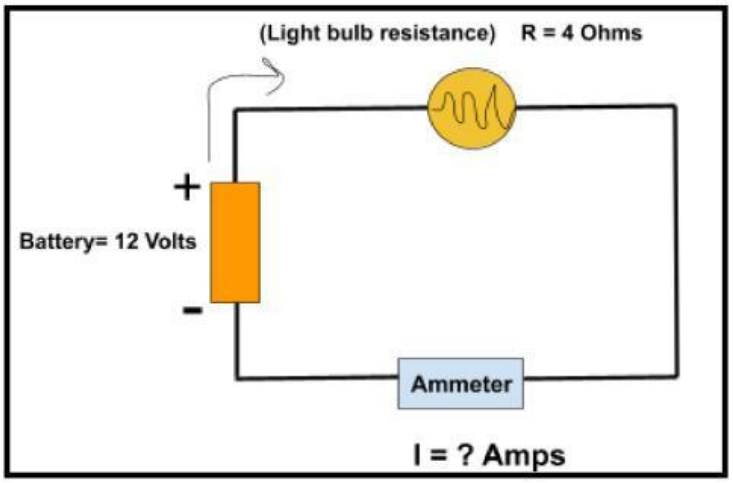


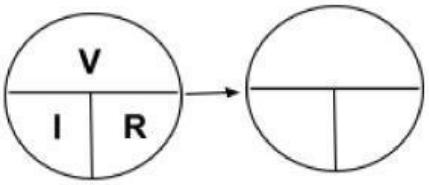What current does the ammeter measure in Amps?




What is the power output of the battery?

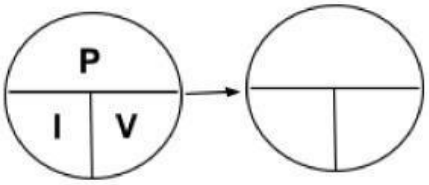


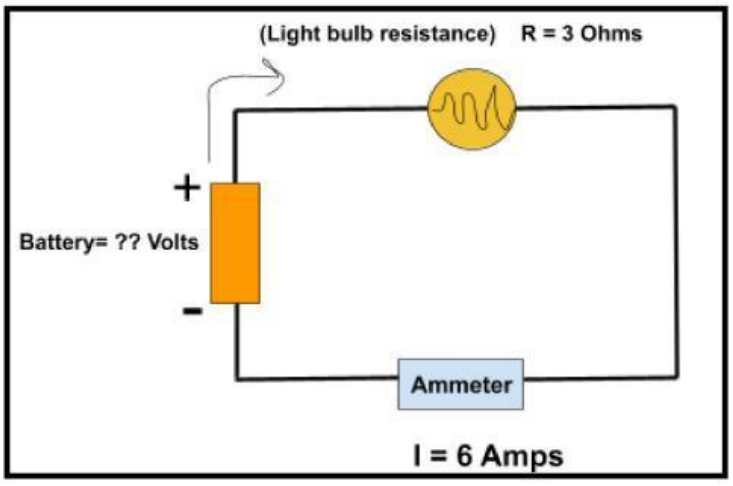


What is the voltage of the battery?

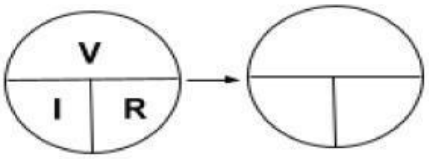


What is the power output of the battery?

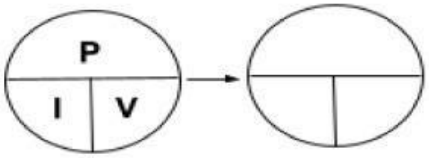


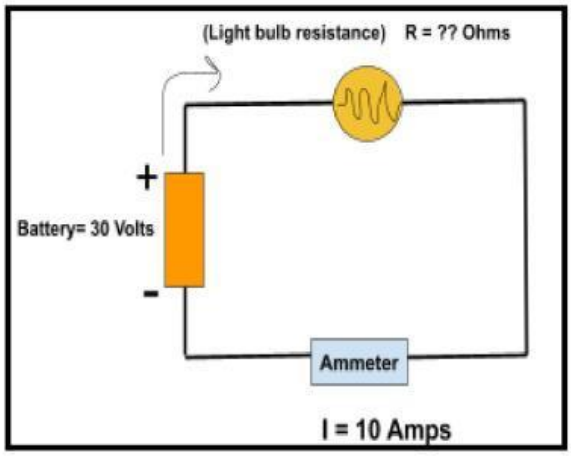

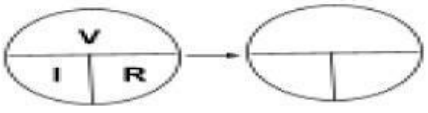What is the resistance of the light bulb in ohms?



What is the power output of the battery?

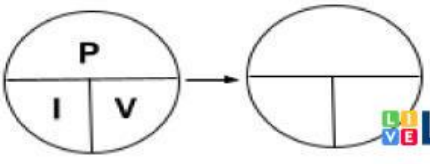

LIVEWORKSHEETS