Circuits

Fill in the missing words

loop | complete | energy | path | negative | positive | electricity

A circuit is a _ _ _ _ _ that allows _ _ _ _ _ _ _ _ _ _ _ _ _ _ _
to pass through it.

Electricity always travels from the _ _ _ _ _ _ _ _ _

to the _ _ _ _ _ _ _ _.

A circuit will only work if it is _ _ _ _ _ _ _ _ _. This means it must make a complete _ _ _ _ _, otherwise the electrical _ _ _ _ _ _ _ cannot flow.

Draw arrows on the diagram to show which way round the electricity is flowing.



LIVEWORKSHEETS