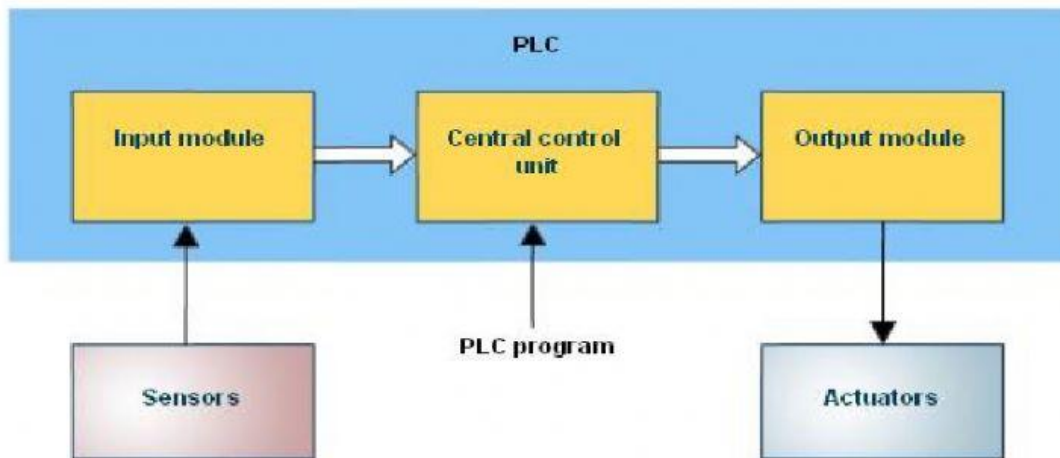


PLC worksheet 1

Fill in the diagram



Identify PLC inputs and outputs.

