
Nusa Jaya School 2021


Year 3A


Date:


TOPIC: Using a switch

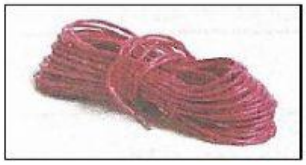(1)Match part of the electric circuits below with their correct names.



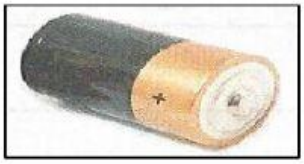

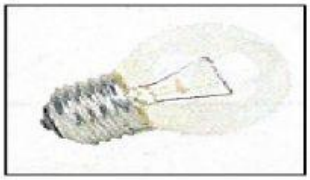

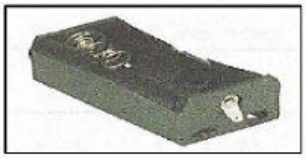



light bulb holder
dry cell holder
light bulb
wires
dry cell

LIVEWORKSHEETS

(2) What happened when you turned the switch to the 'on' position? Why did this happen?

(3) What happened when you turned the switch to the 'off' position? Why did this happen?

(4) What is a switch used for?

LIVEWORKSHEETS