Activity 9

Theory

Look at these circuit diagrams. Which will work? Which need repairs?

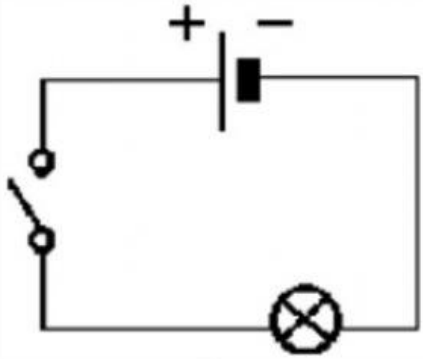

Bulb On	Bulb Off

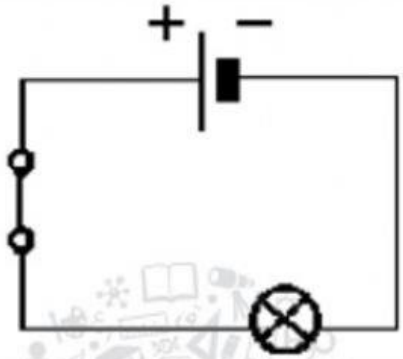

Bulb On	Bulb Off

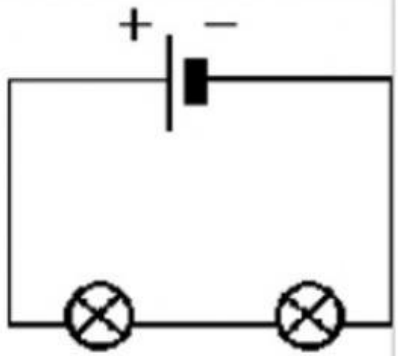

Bulb On	Bulb Off

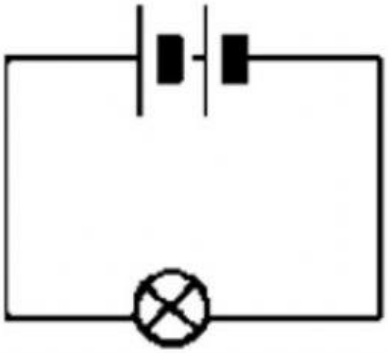

Bulb On	Bulb Off

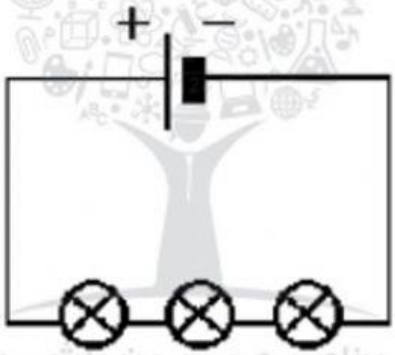

Bulb On	Bulb Off

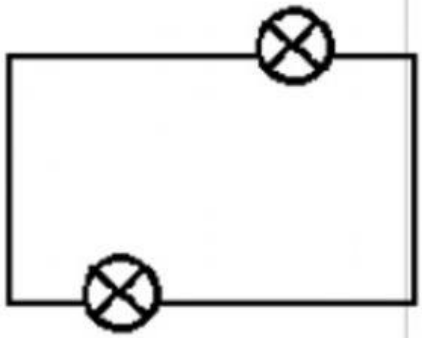

Bulb On	Bulb Off

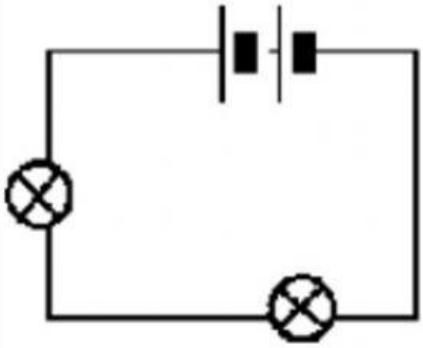

Bulb On	Bulb Off

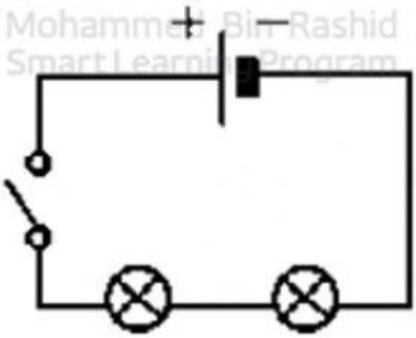

Bulb On	Bulb Off

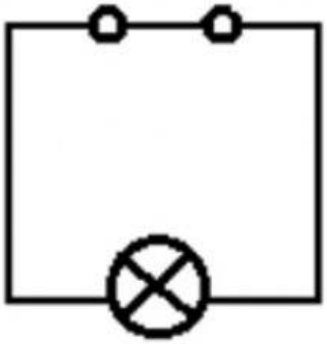

Bulb On	Bulb Off

Mohammed Bin Rashid Smart Learning Program

Copyright © Ministry of Education – United Ar

LIVEWORKSHEETS