

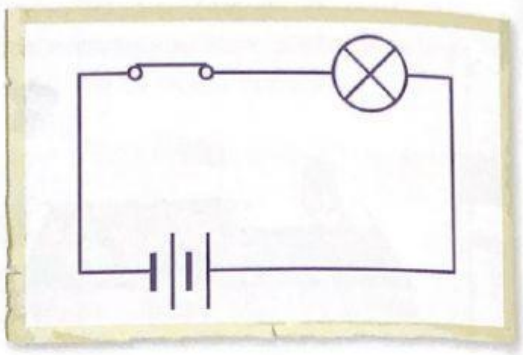
❷ Draw lines to connect the circuit to the correct circuit diagram.




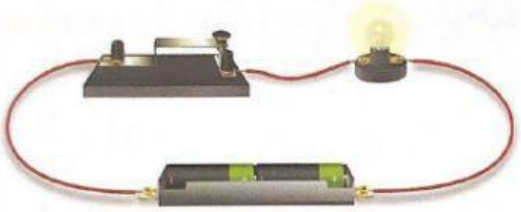


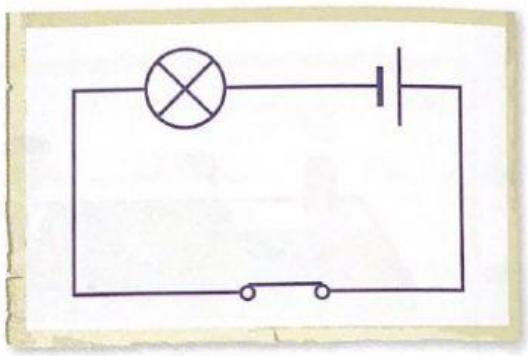






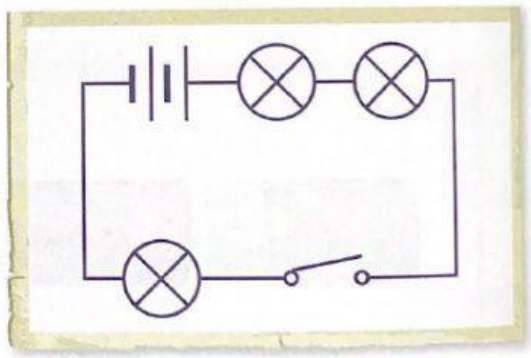

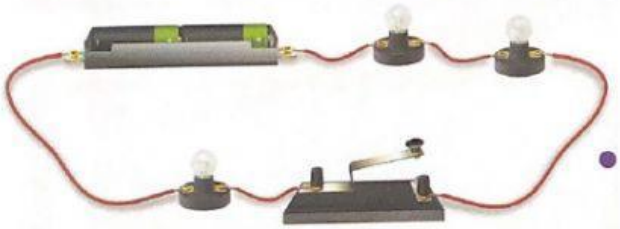

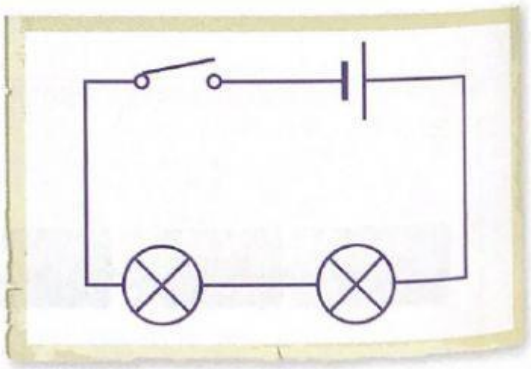

LIVEWORKSHEETS