Write your name and your grade _____

Select the name of the following components




Lamp

Cable

Battery

resistor

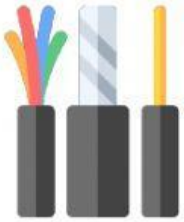

Lamp

Cable

Switch

resistor



Lamp

Short circuit

Battery

cable



energy

bumb

Battery

cable



Lamp

Short circuit

light

cable



line


cable

switch

circuit


LIVEWORKSHEETS

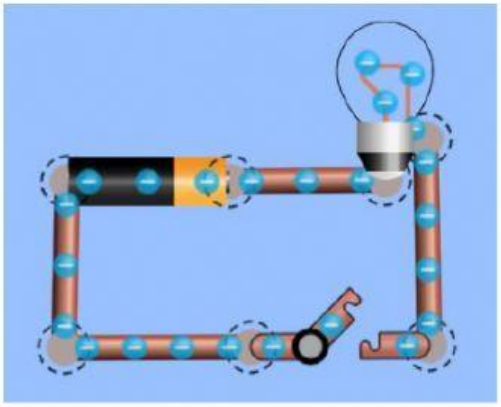Select if the circuit are series circuit or parallel circuit




Series

parallel

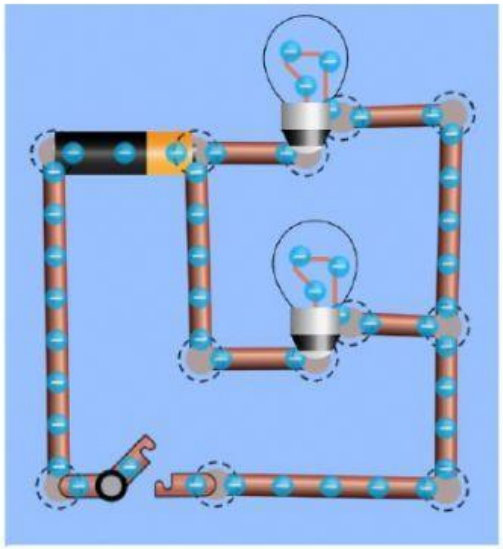


Series

parallel

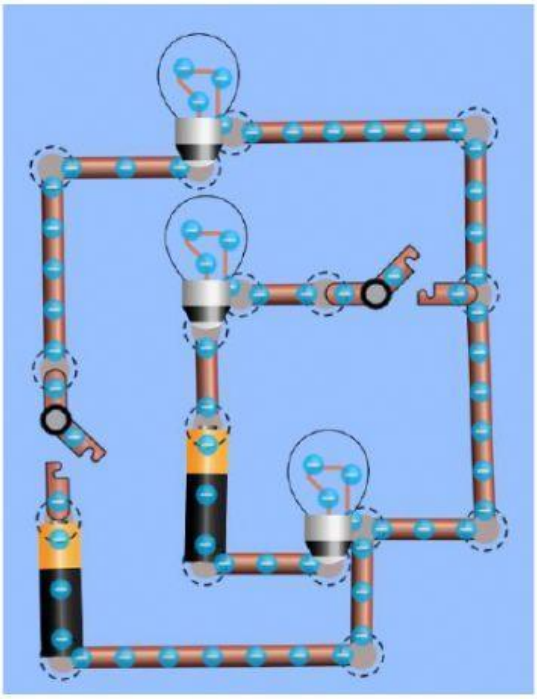

Series

parallel

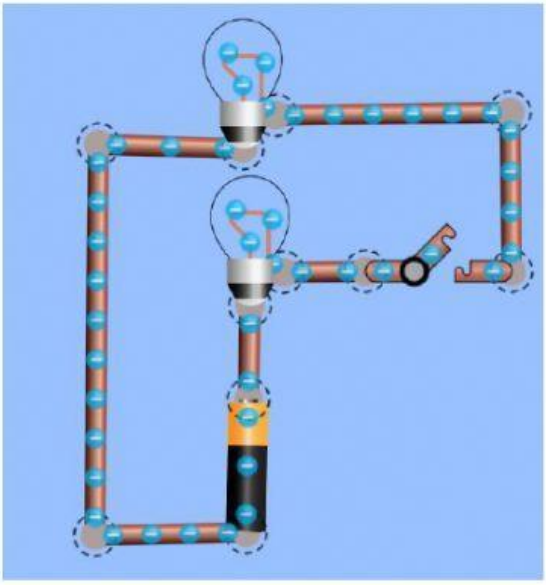

Series

parallel

LIVEWORKSHEETS