What is My Function?

Date:

Activity 3

Match the pictures to their functions.

1. 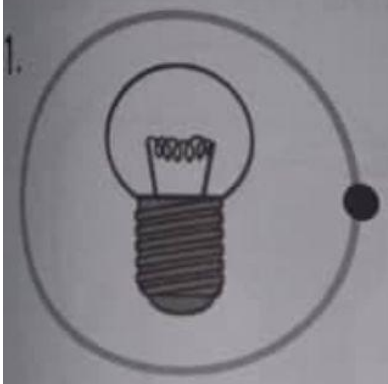

2. 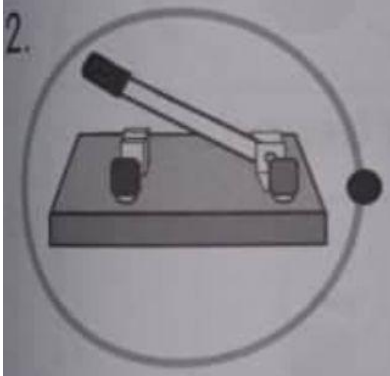

3. 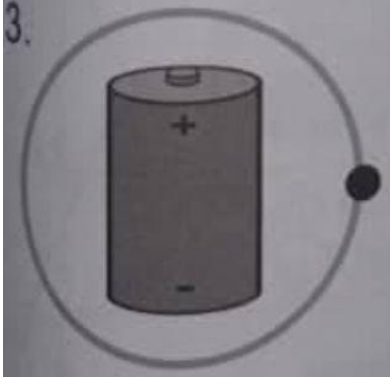

4. 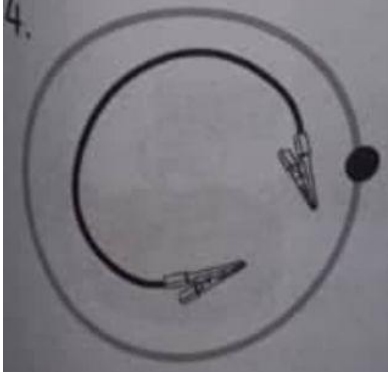

- Supply electrical energy
- Produce light
- Connect components in the electric circuit
- Complete and break the electric circuit

Textbook Page: 76