


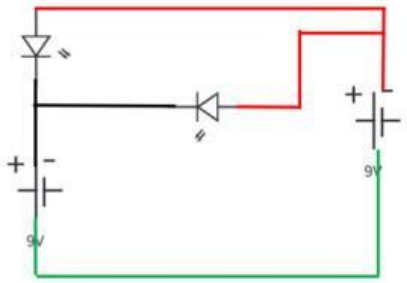
Match each electrical circuit to its schematic representation



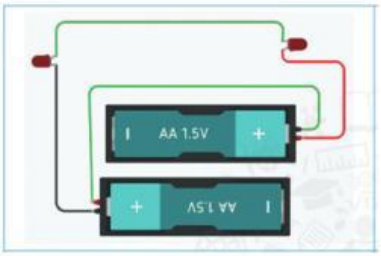

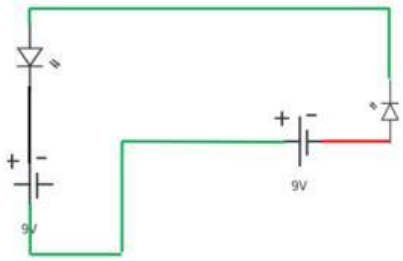

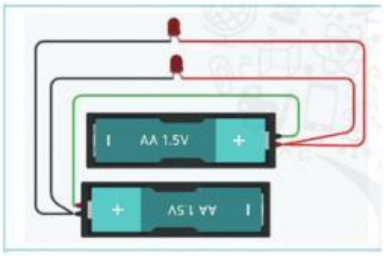

LIVEWORKSHEETS