CIRCUITS

Components of a circuit and their symbols

(Thành phần một mạch điện và ký hiệu của chúng)

**components = parts*

Component	Picture	Symbol	Function
			makes light using electricity
	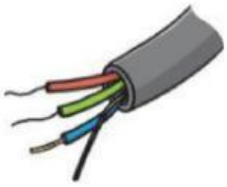		connects components together
	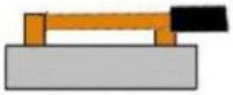		turns the circuit / the light on
	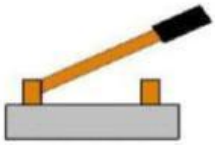		turns the circuit / the light off
			gives energy or provides power

LIVEWORKSHEETS

Answer these questions

CIRCUITS

1.Which component makes light using electricity?

_____

2.Which component gives energy or provides power?

_____

3.Which component connects other components together?

_____

4.Which component turns the circuit / the light off?

_____

5.Which component turns the circuit / the light on?

_____

6.Which one is a complete circuit?

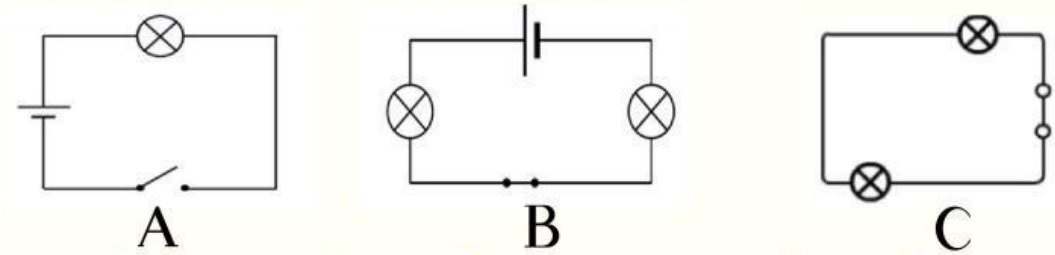

7.Which one is an incomplete circuit?

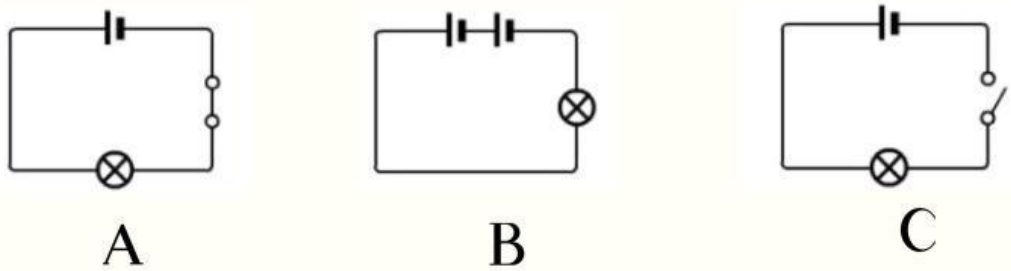

LIVEWORKSHEETS