Unit 5 Electricity

Simple	Series	Open circuit	Parallel

Fill in the Blanks with the correct words

1. A _____ circuit has 2 or more blubs connected to path of a single series.


2. A _____ circuit has two or more paths for current to flow through.
3. A _____ circuit has only one blub connected to path that an electric current travels on.

4. A circuit that is broken is called an _____.


Match the following



SERIES CIRCUIT

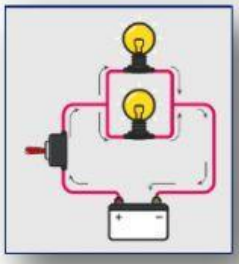

PARALLEL CIRCUIT

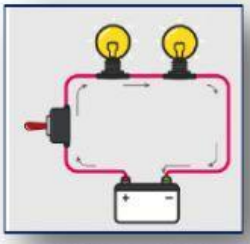


OPEN CIRCUIT

MS POONAM

LIVEWORKSHEETS


IDENTIFY THE COMPONENTS

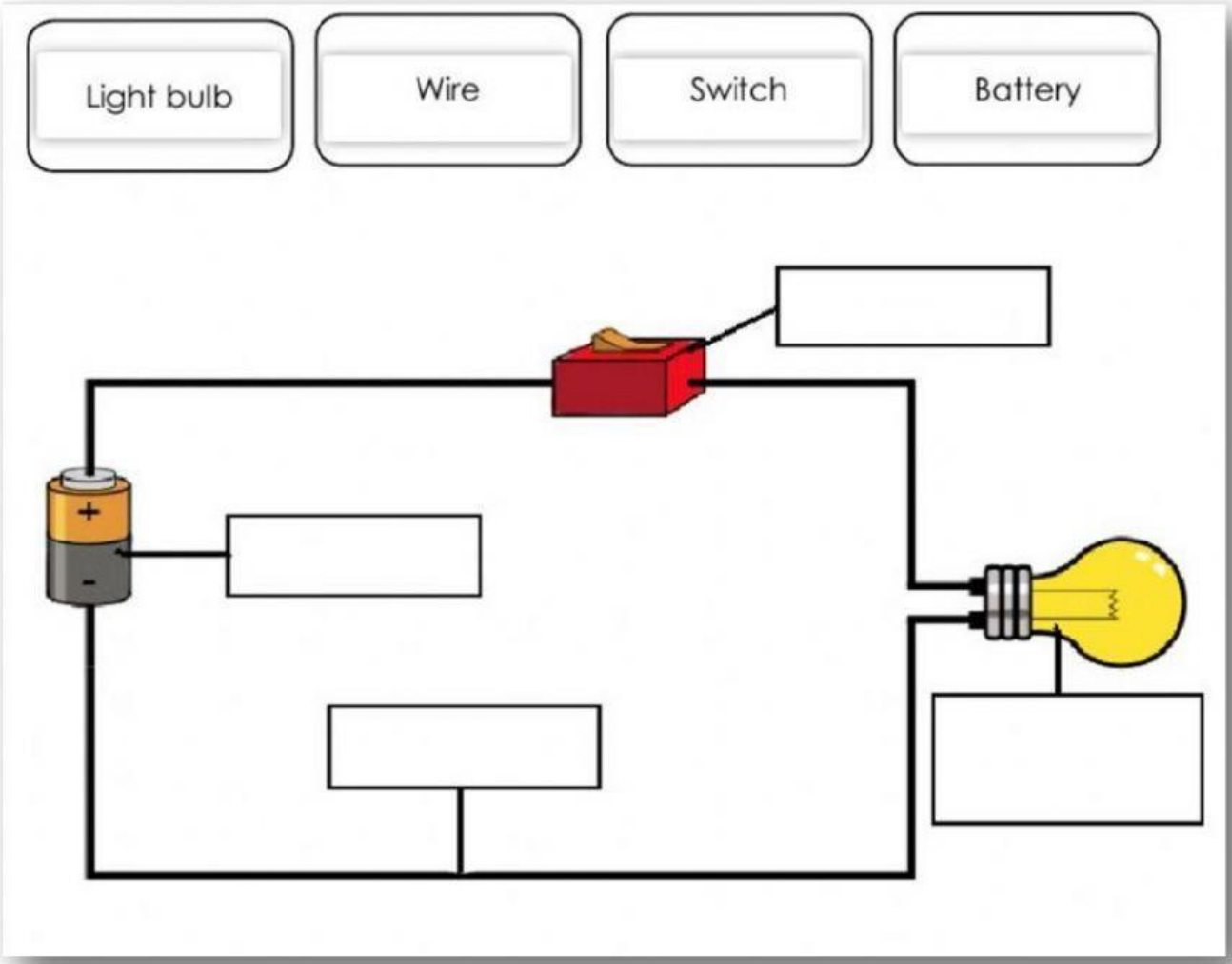

MS POONAM


LIVEWORKSHEETS

Select the correct option

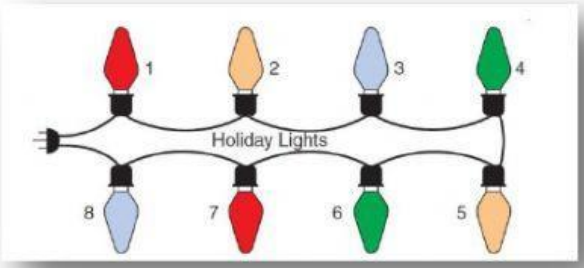

These lights are examples of SERIES CIRCUIT

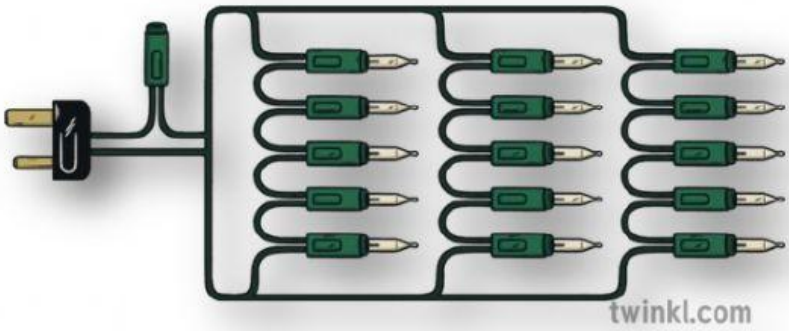These lights are examples of PARALLEL CIRCUIT



These lights are examples of SERIES CIRCUIT

These lights are examples of PARALLEL CIRCUIT

MS POONAM

LIVEWORKSHEETS